



# KHULNA UNIVERSITY OF ENGINEERING & TECHNOLOGY

## KUET

### SESSIONAL REPORT

Course No. EEE-1108  
Department Of Computer Science and Engineering

Experiment No. 03

Name of the Experiment Verification of Superposition theorem

Remarks

*MD SHANJID AREFIN*

Date of Performance 11 Feb 2019

Date of Submission 18 Feb 2019

Name MD SHANJID AREFIN

Roll No H0 1807104

Group No B2 ~~A3~~

Year 1st

Semester 1st

## 1.0 Objectives:

By performing this experiment, various things will be known. The purpose of the experiment are -

1. To gather knowledge about superposition theorem.
2. To know the connection of the circuit.
3. To describe about applying superposition theorem to both current and voltage levels.
4. To become familiar with its unique ability to separate the impact of each source on the quantity of interest.
5. To verify superposition theorem and be able to apply it.

## 2.0 Introduction:

The superposition theorem is undoubtedly one of the most powerful in the electric field states, "The current through, or voltage across, any element of a network is equal to the algebraic sum of the currents or voltages produced independently by each source."

In other words, this theorem allows us to find a solution for a current or voltage using only one



source at a time. Once we have the solution for each source, we can combine the results to obtain the total solution. The term algebraic in the above theorem appears because the current resulting from the sources of the network can have different directions, just as the resulting voltages can have opposite polarities. As we can consider electrical current an electrical quantity, it can be easily assumed that total current follows through the branch is nothing but the summation of all individual currents contributed by the each individual voltage or current source. This conception mathematically represents the superposition theorem.

## 3.0 Apparatus Required:

SL	Name of Apparatus	Specifications	Quantity
1	DC Power Supply	0-30V	2
2	Ammeter	0-1A	1
3	Turnbale Switch	6A-220V	3
4	Connecting Wires	—	as required
5	Volt Meter	0-50V	1
6	Rheostat	21.5Ω, 101.4Ω 63.4Ω	3

#### E 4.0 Experimental Setup:

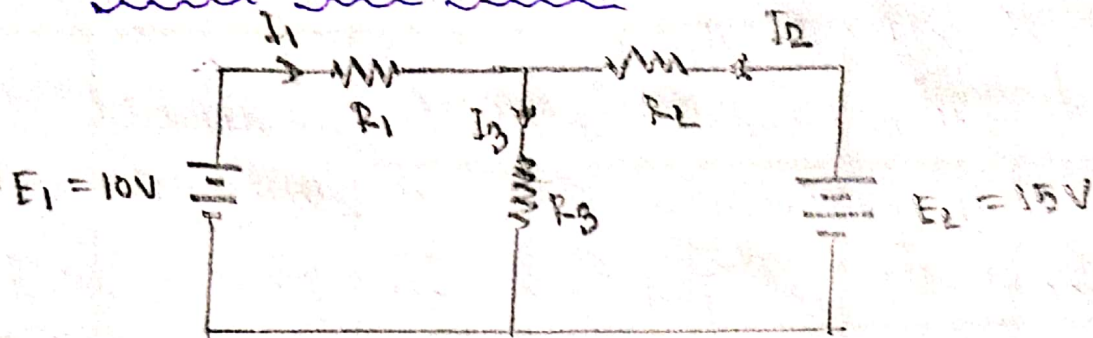


Fig. 4.1 :  $E_1$  (active) and  $E_2$  (active)

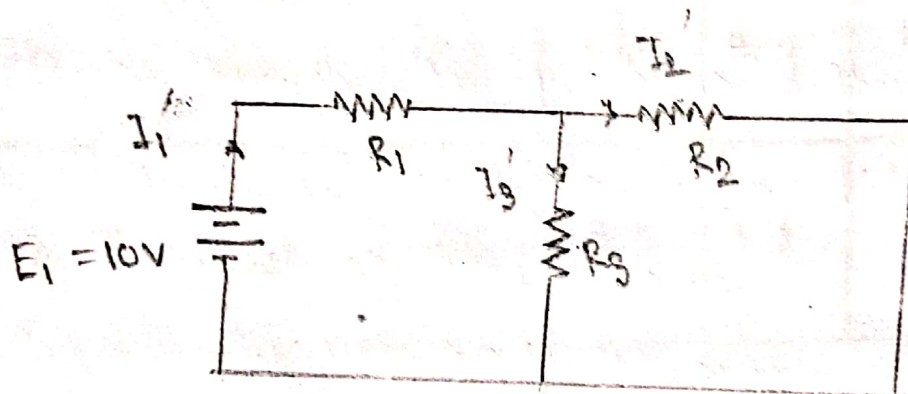


Fig. 4.2 :  $E_1$  (active) and  $E_2$  (inactive)

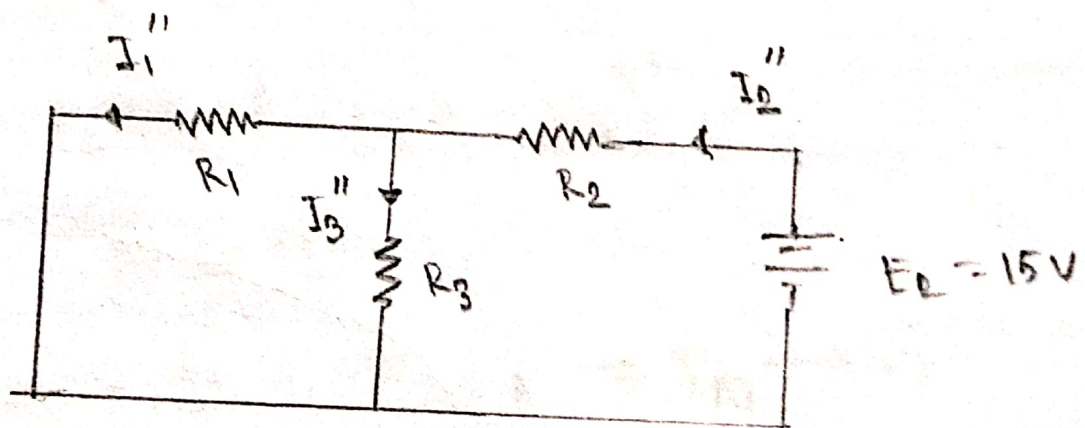


Fig. 4.3 :  $E_1$  (inactive) and  $E_2$  (active)



## 5.0. Experimental Data Table:

SL	Source condition	Voltage (Volt)			Current I (A)		
		V <sub>1</sub>	V <sub>2</sub>	V <sub>3</sub>	I <sub>1</sub>	I <sub>2</sub>	I <sub>3</sub>
01	E <sub>1</sub> active E <sub>2</sub> inactive	3.5	6.5	6.5	0.16	0.06	0.10
02	E <sub>1</sub> inactive E <sub>2</sub> active	3.4	1.6	3.4	0.15	0.17	0.03
03	E <sub>1</sub> active E <sub>2</sub> active	0.1	5.2	9.8	0.01	0.08	0.08

## 6.0 calculation:

□ When E<sub>1</sub> is in the circuit. (10V)

$$R_T = 21.5 + \left( \frac{1}{63.4} + \frac{1}{101.4} \right)^{-1} \Omega$$

$$= 60.0094 \Omega$$

$$I_{AB_1} = \frac{E_1}{R_T} = \frac{10}{60.0094} \text{ A} \Rightarrow I_{AB} = 0.167$$

$$I_{BC_1} = \frac{R_3}{R_2 + R_3} \times I_{AB_1} = \frac{101.4}{101.4 + 63.4} \times 0.167 = 0.1027 \text{ A}$$

$$I_{BD_1} = \frac{R_2}{R_2 + R_3} \times I_{AB_1} = \frac{63.4}{101.4 + 63.4} \times 0.167 = 0.06 \text{ A}$$

Q1 When  $E_2$  is in the circuit (15V)

$$R_T = R_2 + \left( \frac{1}{R_1} + \frac{1}{R_3} \right)^{-1}$$

$$= 63.4 + \left( \frac{1}{21.5} + \frac{1}{101.4} \right)^{-1} = 81.138 \Omega$$

$$I_{BC_2} = \frac{E_2}{R_T} = \frac{15}{81.138} = 0.17 \text{ A}$$

$$I_{AB_2} = \frac{101.4 \times 0.17}{21.5 + 101.4} = 0.15 \text{ A}$$

$$I_{BD_2} = \frac{21.5 \times 0.17}{101.4 + 21.5} = 0.03 \text{ A}$$

Calculated current;

$$I_{AB} = 0.01 \text{ A} \quad I_{BC} = 0.08 \text{ A}, \quad I_{BD} = 0.08 \text{ A}$$

Percentage of error:

$$\% E = \frac{I_m - I_c}{I_m} \times 100 \%$$



$$\begin{aligned}\% E_{AB} &= \frac{0.01 - 0.01}{0.01} \times 100\% \\ &= 0\%\end{aligned}$$

$$\begin{aligned}\% E_{BC} &= \frac{0.11 - 0.08}{0.11} \times 100\% \\ &= 27.27\%\end{aligned}$$

$$\begin{aligned}\% E_{BD} &= \frac{0.08 - 0.07}{1.00} \times 100\% \\ &= 12.5\%\end{aligned}$$

### 7.0 Discussion :

They were some errors which were found in the experiment but it <sup>hadn't</sup> ~~didn't~~ created a big difference between calculated value and measured value. The error values were 0%, 27.27%, 12.5% in respect. The cause of these errors was the temperature effect as well as

the fractional values in the ammeter. The value of the resistance might have changed due to temperature. The procedure could have been a little better.

8.0 Conclusion: By completing this experiment we came to know about the verification of superposition theorem. ~~Various~~ The theory allowed us to obtain a solution of measuring current and voltage at a time combining the result of both perspective. Though there was a slight error during the procedure being done, we verified the superposition theorem properly.

9.0 References: 1. "Introductory Circuit Analysis" — Robert L. Boylestad  
2. Google 3. Wikipedia